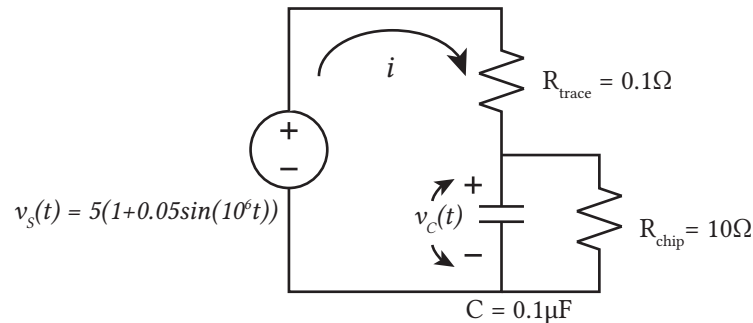


## Homework 2

Due: September 13, 2020

Name:

1. (20 points) We have a power supply  $v_s$  which is powering a chip. The power supply nominally generates 5V, but it also has a 1MHz ripple. There is a PCB trace (wire) connecting the power supply to the chip which has a small resistance  $R_{trace} = 0.1\Omega$ . We can model the chip which is drawing power from the resistor as  $R_{chip} = 10\Omega$ . To reduce the supply ripple, we put a decoupling capacitor next to the chip.



- (5 points) Write Kirchoff's Current law for the ground node in this circuit.
- (10 points) Write Kirchoff's Voltage Law equation for the two loops (one involving the capacitor and the other involving  $R_{chip}$ ).
- (10 points) Combine the equations from parts a and b into one where the only unknown is  $v_{chip}$ .
- (5 points) Put the equation from part c into standard form for an integrating factor  $\frac{df}{dt} + Pf(t) = Q$
- (5 points) Write out the integrating factor  $I = e^{\int P dt}$
- (5 points) Multiply the equation from part d by the integrating factor.
- (5 points) Solve the differential equation from part (f) for  $v_{chip}(t)$ :

$$If(t) = \int IQ dt$$

- (5 points) Plot the solution from part (g).